

**Series and Parallel**

Sep 4-4:26 PM

Aug 11-2:48 PM

A 12 ohm resistor and a 6 ohm resistor are connected in parallel to a battery, and the current in the 12 ohm resistor is found to be 2 A. Find the potential difference across the battery.

Nov 6-1:37 PM

Sep 4-4:20 PM

A 16 ohm resistor and a 12 ohm resistor are connected in series with a battery. The potential difference across the battery is measured as 14V. Find the potential difference across the 12ohm resistor.

Nov 7-5:40 PM

Sep 4-4:22 PM