

Power

Sep 4-4:26 PM

Power = VI

Sep 4-4:23 PM

A toaster is rated at 800W, and a grill is rated at 1500W. Can I use both at the same time on a single 120V circuit protected with a 20A breaker?

Nov 7-5:42 PM